


POJAČAVAČ SA ZAJEDNIČKIM EMITOROM KAO POJAČAVAČ SNAGE

prepostavljen napon između kolektora i emitora, "izlazni" napon

(%i1) $vce: (Vcc/2)*(1+\sin(wt));$

$$(\%o1) \frac{Vcc (\sin (wt) + 1)}{2}$$

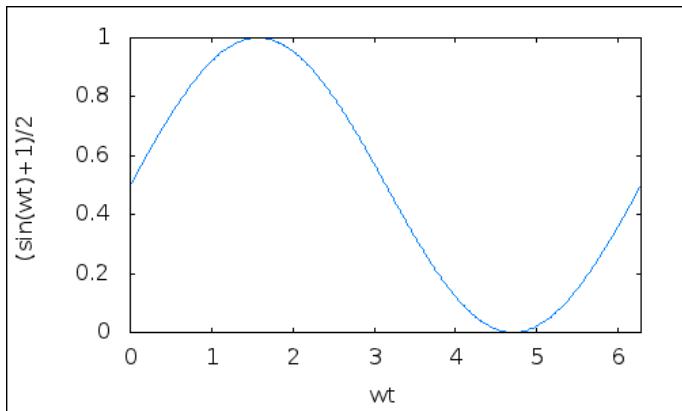(%i2) $wxplot2d(vce/Vcc, [wt, 0, 2*\pi]);$




(%o2)

odgovarajuća struja kolektora

(%i3) $ic: (Vcc/(2*R))*(1-\sin(wt));$

$$(\%o3) \frac{Vcc (1 - \sin (wt))}{2 R}$$

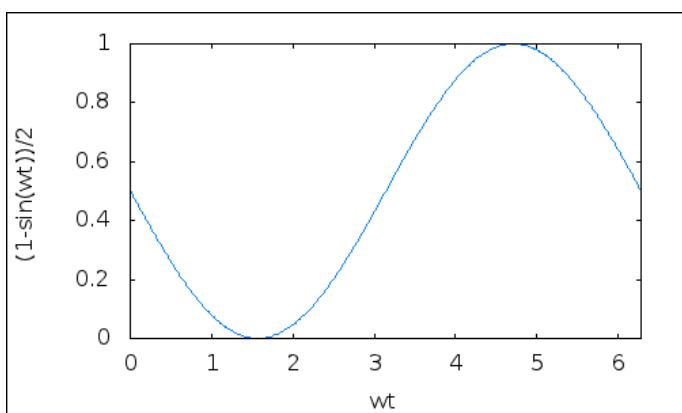(%i4) $wxplot2d(ic/(Vcc/R), [wt, 0, 2*\pi]);$




(%o4)

trenutna snaga disipacije na tranzistoru

(%i5) $pd: vce*ic;$

$$(\%o5) \frac{Vcc^2 (1 - \sin (wt)) (\sin (wt) + 1)}{4 R}$$
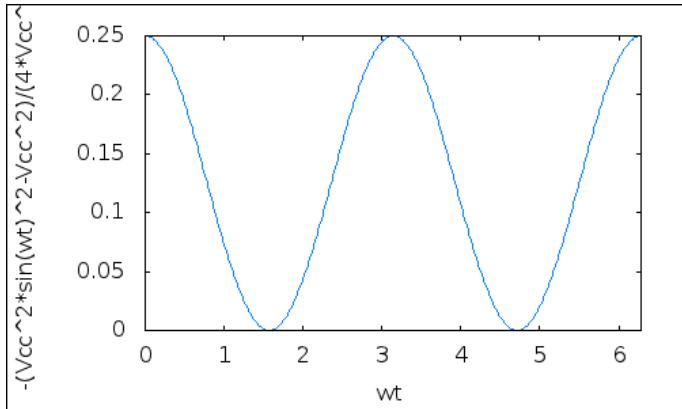
```
(%i6) pd: ratsimp(pd);
(%o6) -  $\frac{V_{cc}^2 \sin(wt)^2 - V_{cc}^2}{4R}$ 
(%i7) wxplot2d(pd/(Vcc^2/R), [wt, 0, 2*pi]);
```



(%o7)

srednja snaga disipacije na tranzistoru

```
(%i8) Pd: 1/(2*pi)*integrate(pd,wt,0,2*pi);
```

$$(\%o8) \frac{V_{cc}^2}{8R}$$

napon na otporniku, KZN


```
(%i9) vr: Vcc-vce;
```

$$(\%o9) V_{cc} - \frac{V_{cc} (\sin(wt) + 1)}{2}$$

```
(%i10) vr: ratsimp(vr);
```

$$(\%o10) - \frac{V_{cc} \sin(wt) - V_{cc}}{2}$$
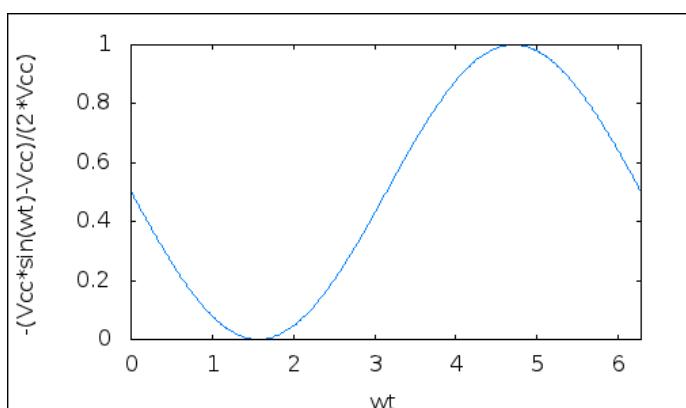
```
(%i11) wxplot2d(vr/Vcc, [wt, 0, 2*pi]);
```



(%t11)

(%o11)

trenutna snaga na otporniku


(%i12) pr: vr*ic;

$$(\%o12) - \frac{V_{cc} (1 - \sin(wt)) (V_{cc} \sin(wt) - V_{cc})}{4 R}$$

(%i13) pr: ratsimp(pr);

$$(\%o13) \frac{V_{cc}^2 \sin(wt)^2 - 2 V_{cc}^2 \sin(wt) + V_{cc}^2}{4 R}$$

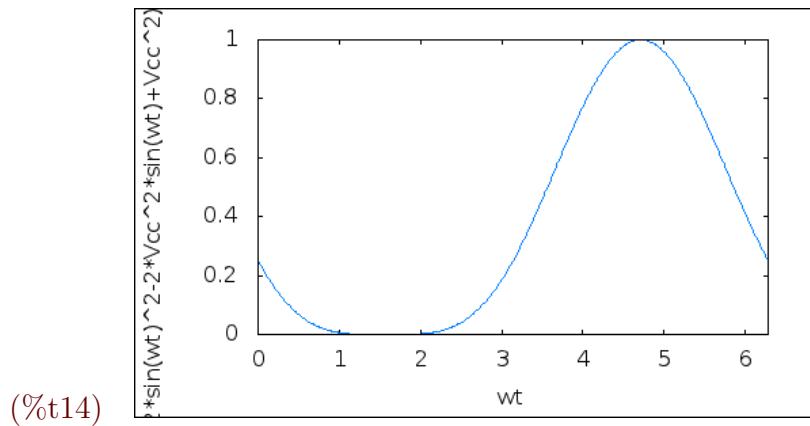(%i14) wxplot2d(pr/(Vcc^2/R), [wt, 0, 2*pi]);



(%o14)

srednja snaga na otporniku

(%i15) Pr: 1/(2*pi)*integrate(pr,wt,0,2*pi);


$$(\%o15) \frac{3 V_{cc}^2}{8 R}$$

trenutna snaga koju izvor za napajanje ulaže u kolo

(%i16) pcc: Vcc*ic;

$$(\%o16) \frac{V_{cc}^2 (1 - \sin(wt))}{2 R}$$

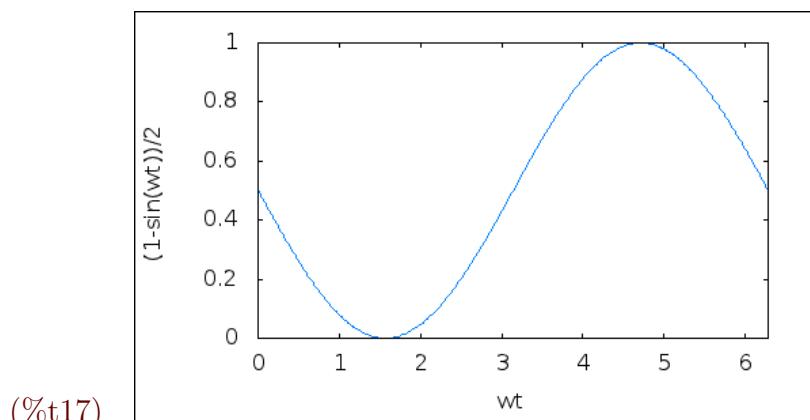(%i17) wxplot2d(pcc/(Vcc^2/R), [wt, 0, 2*pi]);



(%o17)

srednja snaga koju izvor za napajanje ulaže u kolo

(%i18) $P_{cc} := 1/(2*\pi)*\int(p_{cc}, wt, 0, 2*\pi);$

$$(\%o18) \quad \frac{V_{cc}^2}{2R}$$

zakon o održanju energije na nivou trenutne snage

(%i19) $p_{cc}-p_{d};$

$$(\%o19) \quad -\frac{V_{cc}^2 \sin(wt)^2 - 2V_{cc}^2 \sin(wt) + V_{cc}^2}{4R} + \frac{V_{cc}^2 \sin(wt)^2 - V_{cc}^2}{4R} + \frac{V_{cc}^2 (1 - \sin(wt))}{2R}$$

(%i20) $\text{ratsimp}(%);$

$$(\%o20) \quad 0$$

zakon o održanju energije na nivou srednje snage

(%i21) $P_{cc}-P_d-P_r;$

$$(\%o21) \quad 0$$